

Ayisharinsi /  
PCB-Design--Automatic-night-lamp

&lt;&gt; Code

Pull requests

Actions

Projects

Wiki

Security

Insights



main

PCB-Design--Automatic-night-lamp / README.md



Ayisharinsi Update README.md

now



62 lines (35 loc) · 3.44 KB

Preview

Code

Blame

Raw



# PCB-Design--Automatic-night-lamp

## Aim

To design a PCB circuit for automatic night lamp using eagle software.

## Software required

Eagle

## Procedure

Open EAGLE and create a new project for your PCB design.

Open a new schematic file within your project.

Use the libraries provided in EAGLE or create custom libraries if necessary.

Place components onto the schematic sheet by using the 'Add' tool.

Connect the components using the 'Net' tool.

Label nets appropriately to ensure clarity

Once routing is complete, perform a ERC to ensure there are no errors and save the schematic.

Click on the 'Generate/Switch to Board' icon to create a board from your schematic.

EAGLE's board layout editor allows you to place components, route traces, and define board shapes.

Arrange components on the board to optimize space usage and minimize signal interference.

Route traces to connect components according to your schematic.

Use the various routing and editing tools provided by EAGLE to ensure proper routing and avoid design rule violations.

Once routing is complete, perform a design rule check (DRC) to ensure there are no errors and save the board layout.

Go to File > CAM Processor and set up CAM jobs to generate Gerber files for your PCB layers.

Verify generated files to ensure they contain all necessary information.

Save the generated manufacturing files

## Theory

---

Here is a simple dark sensor circuit that is useful to switch ON and OFF any appliances automatically depending on the Light. As an output device, we'll utilise an LED in this example. To detect the light, we will use an LDR (Light-dependent Resistor). As the name says, when the light intensity on LDR is high, the resistance through it decreases; when the light intensity on LDR is low, the resistance through it increases and becomes extremely high. It's a kind of variable resistor, but the resistance varies based on the light.


## Working

## Circuit Diagram


[illegible]

## Output

## 3/4

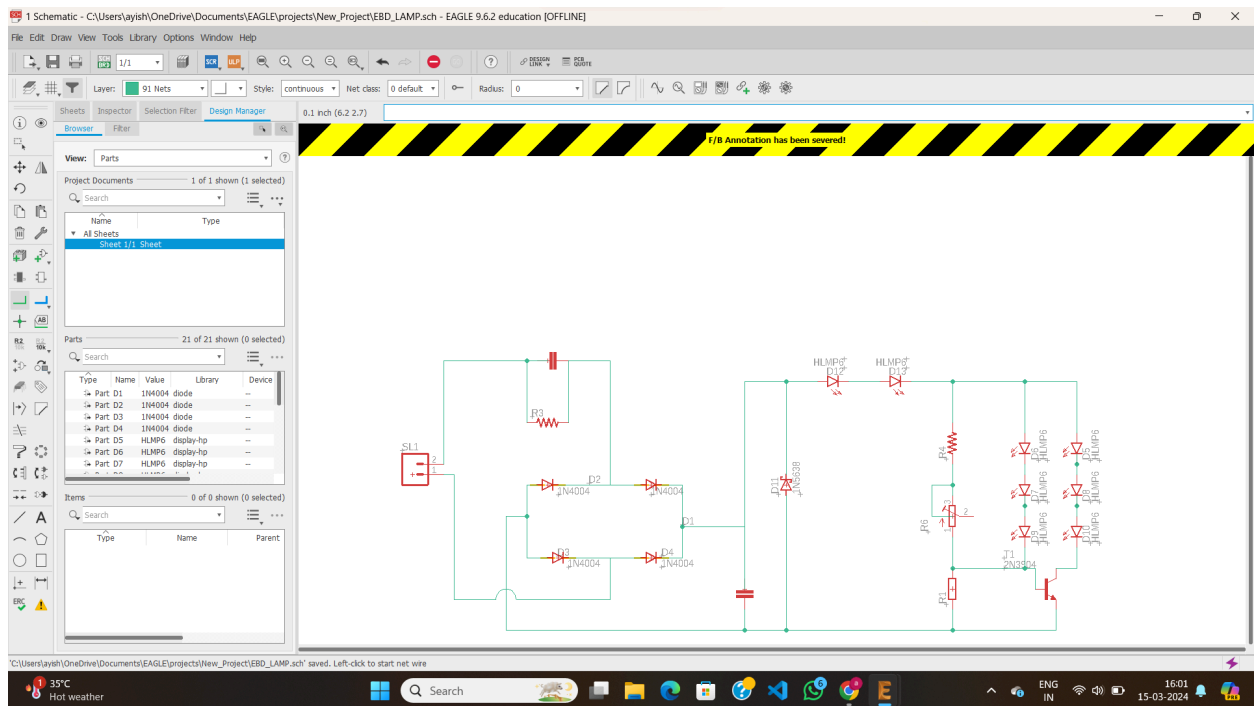

## Layout diagram

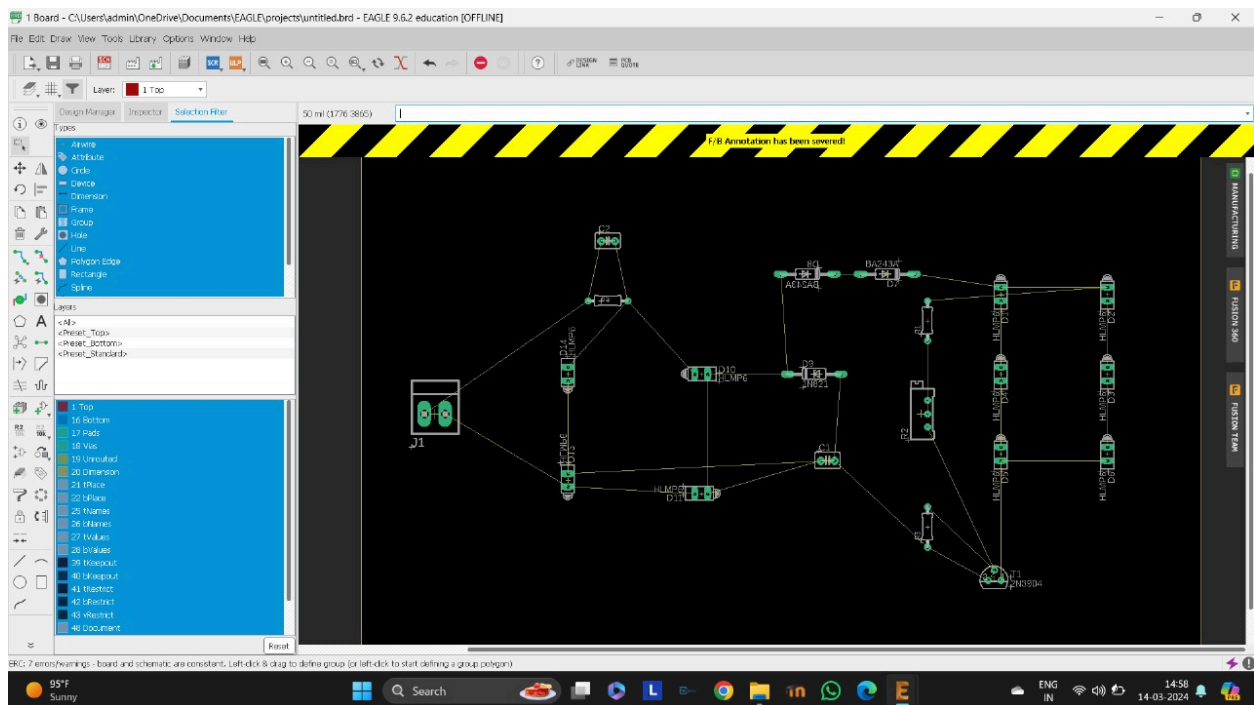

## Result

Thus the automatic night lamp circuit was designed using proteus software.